



```
%Program To calculate Reactive Power Flow Through transmission
```

```
E1=input('Source# 1 Voltage Mag = ');
a1=input('Source# 1 Phase Angle = ');
E2=input('Source# 2 Voltage Mag = ');
a2=input('Source# 2 Phase Angle = ');
R=input('Line Resistance = ');
X=input('Line Reactance = ');
Z= R+ j*X;
E1=(0.75*E1:1:1*E1)';
alr=a1*pi/180;
k=length (E1);
E2=ones(k,1)*E2;
a2r=a2*pi/180;
V1=E1.*cos(alr)+j*E1.*sin(alr);
V2=E2.*cos(a2r)+j*E2.*sin(a2r);
I12=(V1-V2)/Z;
I21=-I12;
S1=V1.*conj (I12);
P1=real (S1);
Q1=imag (S1);
S2=V2.*conj (I21);
P2= real (S2);
Q2=imag (S2);
SL=S1+S2;
PL=real (SL);
QL=imag (SL);
Result1=[E1, Q1, Q2, PL];
disp('E1 Q-1 Q-2 P-L')
```

```
E1 Q-1 Q-2 P-L
```

```
disp (Result1);
```

```
90.0000 392.2008 -392.2008 84.2477
91.0000 396.5586 -396.5586 75.1282
92.0000 400.9164 -400.9164 67.0088
93.0000 405.2742 -405.2742 59.8893
94.0000 409.6320 -409.6320 53.7698
95.0000 413.9898 -413.9898 48.6504
96.0000 418.3476 -418.3476 44.5309
97.0000 422.7054 -422.7054 41.4114
98.0000 427.0631 -427.0631 39.2920
99.0000 431.4209 -431.4209 38.1725
100.0000 435.7787 -435.7787 38.0530
101.0000 440.1365 -440.1365 38.9335
102.0000 444.4943 -444.4943 40.8141
103.0000 448.8521 -448.8521 43.6946
104.0000 453.2099 -453.2099 47.5751
105.0000 457.5676 -457.5676 52.4557
106.0000 461.9254 -461.9254 58.3362
107.0000 466.2832 -466.2832 65.2167
108.0000 470.6410 -470.6410 73.0973
109.0000 474.9988 -474.9988 81.9778
110.0000 479.3566 -479.3566 91.8583
```

111.0000	483.7144	-483.7144	102.7389
112.0000	488.0722	-488.0722	114.6194
113.0000	492.4299	-492.4299	127.4999
114.0000	496.7877	-496.7877	141.3804
115.0000	501.1455	-501.1455	156.2610
116.0000	505.5033	-505.5033	172.1415
117.0000	509.8611	-509.8611	189.0220

```

plot (E1, Q1, E1, Q2, E1, PL);
xlabel('Source# 1 Voltage Magnitude =');
ylabel('Q, Var')
text (-26, -550, 'Q1'),
text(-26,600,'Q2'),
text(-26, 100, 'PL')

```

