


```
%Program To calculate Reactive Power Flow Through transmission
```

```
E1=input('Source# 1 Voltage Mag = ');
a1=input('Source# 1 Phase Angle = ');
E2=input('Source# 2 Voltage Mag = ');
a2=input('Source# 2 Phase Angle = ');
R=input('Line Resistance = ');
X=input('Line Reactance = ');
Z= R+ j*X;
E1=(0.75*E1:1:1*E1)';
alr=a1*pi/180;
k=length (E1);
E2=ones(k,1)*E2;
a2r=a2*pi/180;
V1=E1.*cos(alr)+j*E1.*sin(alr);
V2=E2.*cos(a2r)+j*E2.*sin(a2r);
I12=(V1-V2)/Z;
I21=-I12;
S1=V1.*conj (I12);
P1=real (S1);
Q1=imag (S1);
S2=V2.*conj (I21);
P2= real (S2);
Q2=imag (S2);
SL=S1+S2;
PL=real (SL);
QL=imag (SL);
Result1=[E1, Q1, Q2, PL];
disp('E1 Q-1 Q-2 P-L')
```

```
E1 Q-1 Q-2 P-L
```

```
disp (Result1);
```

90.0000	392.2008	-392.2008	84.2477
91.0000	396.5586	-396.5586	75.1282
92.0000	400.9164	-400.9164	67.0088
93.0000	405.2742	-405.2742	59.8893
94.0000	409.6320	-409.6320	53.7698
95.0000	413.9898	-413.9898	48.6504
96.0000	418.3476	-418.3476	44.5309
97.0000	422.7054	-422.7054	41.4114
98.0000	427.0631	-427.0631	39.2920
99.0000	431.4209	-431.4209	38.1725
100.0000	435.7787	-435.7787	38.0530
101.0000	440.1365	-440.1365	38.9335
102.0000	444.4943	-444.4943	40.8141
103.0000	448.8521	-448.8521	43.6946
104.0000	453.2099	-453.2099	47.5751
105.0000	457.5676	-457.5676	52.4557
106.0000	461.9254	-461.9254	58.3362
107.0000	466.2832	-466.2832	65.2167
108.0000	470.6410	-470.6410	73.0973
109.0000	474.9988	-474.9988	81.9778
110.0000	479.3566	-479.3566	91.8583

111.0000	483.7144	-483.7144	102.7389
112.0000	488.0722	-488.0722	114.6194
113.0000	492.4299	-492.4299	127.4999
114.0000	496.7877	-496.7877	141.3804
115.0000	501.1455	-501.1455	156.2610
116.0000	505.5033	-505.5033	172.1415
117.0000	509.8611	-509.8611	189.0220

```

plot (E1, Q1, E1, Q2, E1, PL);
xlabel('Source# 1 Voltage Magnitude =');
ylabel('Q, Var')
text (-26, -550, 'Q1'),
text(-26,600,'Q2'),
text(-26, 100, 'PL')

```

